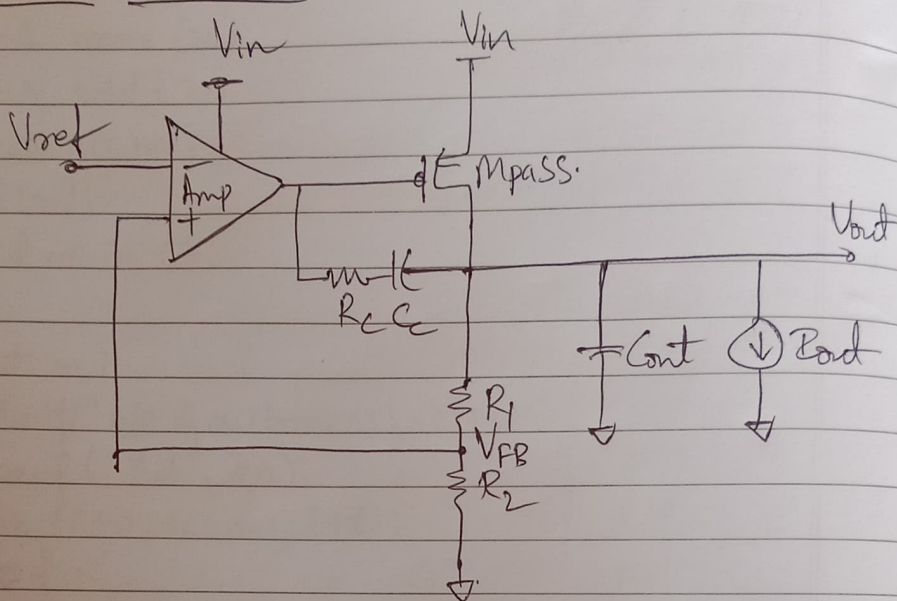


13/05/24

नमो लक्ष्मीनारायण

# Design of LDO (Low Dropout Voltage Regulator)

Overall schematic



$$V_{out} = V_{FB} = \frac{V_{out} \times R_2}{R_1 + R_2}$$

$$\frac{V_{out}}{V_{FB}} = \frac{R_1 + R_2}{R_2} = 1 + \frac{R_1}{R_2}$$

$$\Rightarrow \frac{R_1}{R_2} = \frac{V_{out}}{V_{FB}} - 1$$


For simplicity let's take  $R_1 = R_2$  we get  
 $\frac{V_{out}}{2} = V_{FB}$

$$\text{here } V_{out} = 1.35V$$

$$\text{So } V_{FB} = 0.675V$$

$\Rightarrow$  Pole zero Analysis is posted in the other notes, so kindly Refer that

So from the Pole zero Analysis &

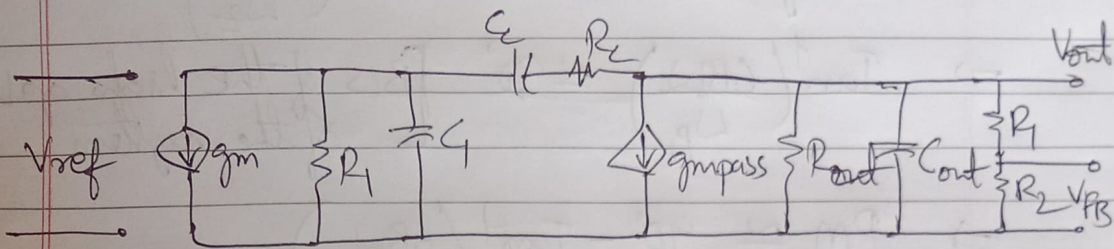

### Small Signal Analysis

$$TF = \frac{-A_1 A_2 (1 - s/\omega_z)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$\omega_{p1} = \frac{1}{R_1 (C_{gpass} + C_c (A_2 + 1))}$$

[We cannot neglect  $C_{gg}$  bcs its in order of 20-80 pF]

$$\omega_{p2} = \frac{1}{C_{out} R_{out}}$$

$$A_2 = -g_{mpass} R_{out}$$

$$A_1 = g_{m1} R_1$$

$$\omega_z = \frac{1}{(1/g_{mpass} - R_2) C_c}$$

For a Phase Margin (P.M)  $\geq 60^\circ$

We need to choose Miller Cap carefully

$$P.M = 180^\circ - \tan^{-1}\left(\frac{GBW}{\omega_z}\right) - \tan^{-1}\left(\frac{GBW}{\omega_{p1}}\right) - \tan^{-1}\left(\frac{GBW}{\omega_{p2}}\right)$$



→ Assuming you to try to neutralize to  $\omega_z$  with nulling resistor the  $\tan^{-1}\left(\frac{GBW}{\omega_z}\right) \approx 0$

→  $\tan^{-1}\left(\frac{GBW}{\omega_{p1}}\right) \approx 90^\circ$  [B.C of the high gain of the system]

$$\Rightarrow PM \approx 90^\circ - \tan^{-1}\left(\frac{GBW}{\omega_{p2}}\right)$$

So we use Miller Compensation to split the  $\omega_{p1}$  &  $\omega_{p2}$  far apart

From this we try to estimate  $C_c$

For spec of  $PM \geq 60^\circ$

$$60^\circ = 90^\circ - \tan^{-1}\left(\frac{GBW}{\omega_{p2}}\right)$$

$$\tan^{-1}\left(\frac{GBW}{\omega_{p2}}\right) \approx 30^\circ$$

For ~~GBW~~  $\frac{GBW}{\omega_{p2}} = 0.577$


$$GBW = \frac{g_{m1}}{C_c} \quad \& \quad \omega_{p2} = \frac{g_{m2}}{C_{out}} \quad \left[ \begin{array}{l} \text{This is approximating} \\ \text{tion needs} \\ \text{tuning} \end{array} \right]$$

We get  $C_c \geq 0.3 C_L$

So for simplicity lets consider  $C_c \approx 30pF$

## Error Amplifier:-

I've used ST-OTA

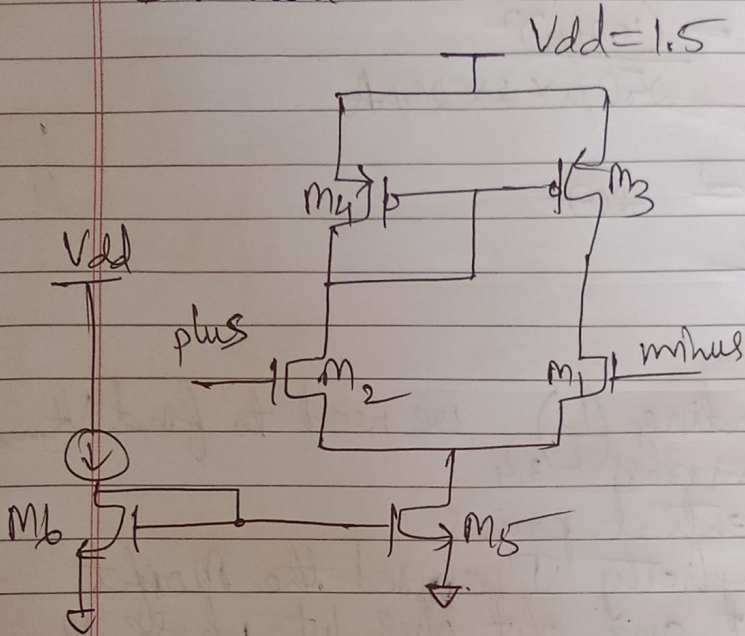

→ Note! I've not used  $g_m/I_d$

Gain  $\geq 40\text{dB}$

$V_{dd} = 1.5\text{V}$

$ICMR^- = 0.75$

$ICMR^+ = 1.2$

$PM \geq 60^\circ$

$C_L = 50\text{pF}$  (I'm considering  $(g_{m,pass} + C_L)$ )

$SR = 1\text{V}/\mu\text{s}$

$I_{ss} = 50\mu\text{A}$

$M_1, M_2$

$$g_{m1,2} = \frac{2\pi}{f} (GBW \times C_L)$$

$$= 2\pi (5 \times 10^6 \times 50 \times 10^{-12})$$

$$\underline{g_{m1,2} = 157\mu\text{S}}$$



$$\left(\frac{W}{L}\right)_{1,2} = \frac{g_{m1,2}^2}{\mu_n C_{ox} 2I_D}$$

$$= \frac{(1571 \mu)^2}{250 \mu \times 2 \times 25 \mu A}$$


$$\left(\frac{W}{L}\right)_{1,2} = 207$$

M<sub>3</sub>, M<sub>4</sub>


⇒ Before finding  $\left(\frac{W}{L}\right)_{3,4}$  we need to find  $V_{th, max}$  of current mirrors and differential pairs.

⇒ For simplicity I've used the Mosfet nfit\_01v8-1v and pfit\_01v8-1v whose  $V_t$  doesn't change ~~the~~ much over Width or length

⇒  $V_{th, max}$  simulation

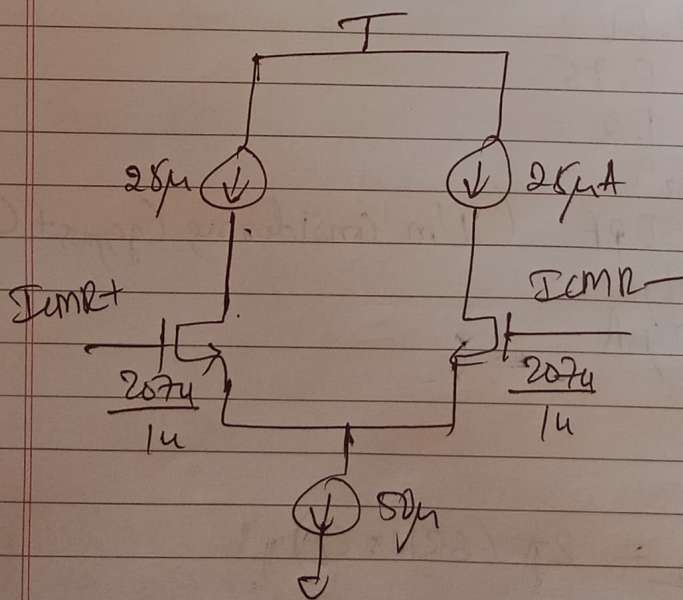

We get  $V_{th, max} = \cancel{0.563563V} 0.48221$   
 $V_{th, min} = \cancel{0.563563V} 0.482106$

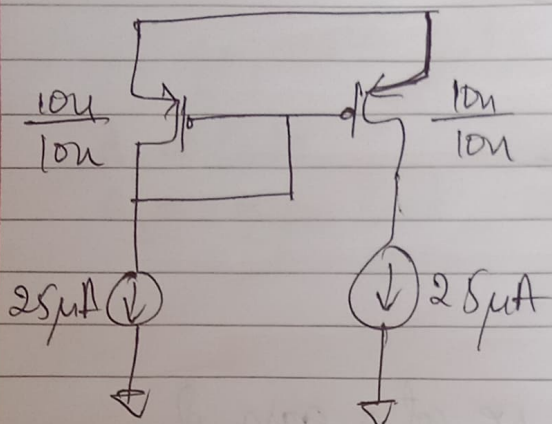$V_{TP3max}$ 

I've put  $\frac{10u}{10n}$   
to avoid short  
channel effects

$$V_{TP3max} = \underline{\underline{0.424058}}$$

$$V_{SG3} = V_{DD} - I_{CMR_{max}} + V_{THmin}$$

$$= 1.5 - 1.2 + 0.482106$$

$$V_{SG3} \approx \underline{\underline{0.8}}$$

$$\left(\frac{W}{L}\right)_{3,4} = \frac{2I_3}{\mu_p \epsilon_0 X (V_{SG3} - V_{TP3max})^2}$$

$$= \frac{50\mu}{55\mu (0.8 - 0.424058)^2}$$

$$\underline{\underline{\left(\frac{W}{L}\right)_{3,4} \approx 7}}$$

M5, M6

$$V_{dsat5} = I_{CMR}(-) - \sqrt{\frac{I_5}{\beta}} - V_{THmin}$$

$$V_{dsat5} \approx \underline{\underline{0.3}}$$

$$\underline{\underline{\left(\frac{W}{L}\right)_{5,6} \approx \frac{50\mu \times 2}{250\mu (0.3)^2} \approx 5}}}$$



$$\left(\frac{W}{L}\right)_{1,2} \approx 207$$

$$\left(\frac{W}{L}\right)_{3,4} \approx 7$$

$$\left(\frac{W}{L}\right)_{5,8} \approx 5$$


Simulating we got a gain of.

$$\text{Gain} : \approx 40\text{dB}$$

$$\text{GBW} : 7\text{MHz}$$

$m_{\text{pass}}$

$$V_{\text{drop}} = |V_{\text{ds}}| = 150\text{mV}$$

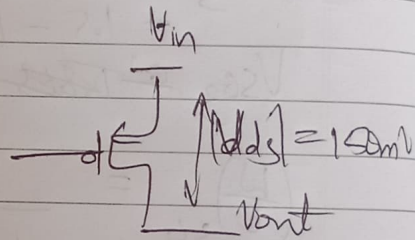

So we target for  $V_{\text{ov}} = 100\text{mV}$

$$I_d = \frac{1}{2} \mu_p C_{\text{ox}} \left(\frac{W}{L}\right)_{\text{pass}} [V_{\text{ov}}]^2$$

$$\left(\frac{W}{L}\right)_{\text{pass}} \approx \frac{2I_n}{\mu_p C_{\text{ox}} [V_{\text{ov}}]^2}$$

$$\left(\frac{W}{L}\right)_{\text{pass}} \approx \frac{2 \times 40 \times 10^{-3}}{55 \times 10^{-6} \times (0.1)^2}$$

$$\left(\frac{W}{L}\right)_{\text{pass}} \approx 145455$$

$$\underline{\underline{C_{\text{ggpass}} \approx 20\text{pF}}}$$

Calculating

$$g_{mpass} \approx \underline{\underline{0.85}}$$

$$A_1 \approx 40\text{dB}$$

$$A_2 = g_{mpass} R_{out} \approx 12 = \underline{\underline{20\text{dB}}}$$

$$\text{Total Gain} \approx 60\text{dB}$$

$$\text{observed Gain} \approx 62\text{dB.}$$

Calculate pole1

$$f_1 = \frac{1}{R_1(C_{gg} + (A_2 + 1)C_c)} \approx \underline{\underline{4\text{kHz (dom)}}}$$

$$f_2 \approx \frac{1}{R_2 C_{out}} \approx \underline{\underline{100\text{MHz (non dom)}}}$$

$$\text{GBW} = \text{AOC} \times \text{Pole1}$$

$$\text{GBW} \approx \underline{\underline{4.8\text{MHz}}}$$

$$\text{P.M} \approx \underline{\underline{80^\circ}}$$

$$\underline{\underline{\text{Efficiency} \approx 89.77\%}}$$